 


**Mount Kenya**



**University**

**UNIVERSITY EXAMINATION 2014/2015**

**SCHOOL OF PURE AND APPLIED SCIENCES  
DEPARTMENT OF ENGINEERING**

**BACHELOR OF SCIENCE LABORATORY TECHNOLOGY  
SCHOOL BASED**

**UNIT CODE: BEG2112**

**UNIT TITLE: BASIC DIGITAL ELECTRONICS AND  
LOGICS**

**DATE: APRIL/MAY 2015**

**MAIN EXAM**

**TIME: 2 HOURS**

**Instructions: Answer Question ONE and ANY other TWO**

**QUESTION ONE (30 MARKS)**

**Question one**

- (a) Distinguish between a digital quantity and an analogue quantity (2mks)
- ✓(b) State one advantage and one disadvantage of synchronous counters over asynchronous counters (2mks)
- ✓(c) Distinguish between sequential logic and combinational logic (2mks)
- (d) An 8-bit digital to analogue converter (DAC) produces  $V_{out}$  of 0.05V for digital input 0000001. Determine both its full scale output and resolution. (2mks)
- (e) Define the following as applied to digital logic families (i)  $V_{OH}(min)$  (ii)  $V_{IH}(min)$  (2mks)
- (f) Convert  $X = (\overline{A} + \overline{B})(A + B + C)$  to standard form. (2mks)

- (g) Draw a logic symbol of a 2-input AND gate and give its truth table. Give a diode circuit implementation of AND gate and sketch output waveform for the input waveforms A and B (4mks)
- (h) Draw a circuit diagram to show how AND gate can be implemented using NOR gates only. (3mks)
- (i) Define the following terms used in combinational logic design: literal, minterm and maxterm. (3mks)
- (j) Explain why CMOS inputs should never be left unconnected (floating)? (3mks)
- (k) Briefly describe how a decoder works. (3mks)
- (l) Define fan-out and fan-in as applied to digital circuits. (2mks)

### **QUESTION TWO (20 MARKS)**

- (a) (i) Convert decimal number 93.347 to binary. (ii) Hexadecimal number  $F3_{16}$  to decimal (iii) Octal number  $7765_8$  to decimal. (3mks)
- (b) Perform the following binary arithmetic (i)  $1101_2 + 1011_2$  (ii)  $00110100_2 - 00001010_2$  (iii)  $1001_2 \times 110_2$  (iv)  $1100_2 \times 011_2$  (4mks)
- (c) Write down the truth table for a three input NAND gate. (3mks)
- (d) Use Boolean Algebra to show that  $(\overline{A}\overline{C}) + A\overline{C} + B.C = B + \overline{C}$  (4mks)
- (e) Sketch the structures of both totem-pole and open collector outputs for TTL devices. (6mks)

### **QUESTION THREE (20 MARKS)**

- (a) Design a logic circuit having three inputs (A, B, C) that will have its output high only when a majority of the input are high. (5mks)
- (b) In digital systems, shift registers are very important components. Draw a block diagram to show how four d-type flip-flops can be converted to form serial in/serial out shift register. (4mks)
- (c) Define fan-out and fan-in as applied to digital circuits. (2mks)
- (d) A74S00 NAND gate has the specified currents:  $I_{OH}=-1\text{mA}$ ,  $I_{IH}=50\mu\text{A}$ ,  $I_{OL}=20\text{mA}$ ,  $I_{IL}=-2\text{mA}$ . Determine the values of fan-out and fan-in for this gate. (3mks)
- (e) By making appropriate substitutions for gates, draw circuits that are equivalent to the one given in figure 5 below using (a) OR gates and invertors only (b) NAND gates and invertors only (6mks)

 


Figure 5.

NAND gates and Invertors

#### **QUESTION FOUR (20 MARKS)**

- (a) Give a logic symbol of SR flip-flop. Explain briefly how it works and derive its truth table. (6mks)
- (b) What is the difference between NOR and the NAND implementation in (4a) above. (2mks)

(c) Use both Boolean algebra and Karnaugh Maps to reduce the following equations to a circuit with the fewest number of gates. (6mks)

(d) Draw up the truth table for the half-adder and show that  $\Sigma = A \oplus B$  and  $C_{out} = A \cdot B$  (3mks)

(e) Show how two half-adders can be interconnected to implement a full-adder. (3mks)

**QUESTION FIVE (20 MARKS)**

(a) (i) Sketch the structures of both totem-pole and open collector outputs for TTL devices. (6mks)

(ii) Briefly explain advantages of a tri-state output stage in (5b) above. (2mks)

(b) Give a block diagram of a half-adder (2mks)

(c) Write the un-simplified minterm Boolean expression for the truth table below and then draw a 4-variable Karnaugh Map. Plot six 1s on the map from the Boolean expression developed. Draw the appropriate loops around groups of 1s on the map. (10mks)

Inputs				Output	Inputs				Output
A	B	C	D	Y	A	B	C	D	Y
0	0	0	0	1	1	0	0	0	0
0	0	0	1	0	1	0	0	1	0
0	0	1	0	0	1	0	1	0	1
0	0	1	1	0	1	0	1	1	1
0	1	0	0	1	1	1	0	0	0
0	1	0	1	0	1	1	0	1	0
0	1	1	0	0	1	1	1	0	1
0	1	1	1	0	1	1	1	1	1

$$\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot D + A \cdot B \cdot C \cdot \bar{D} + A \cdot B \cdot C \cdot D = Y$$

$$Y = BC + A + ABC + AB$$